

PASSWORD SECURITY SYSTEM

A PROJECT REPORT

submitted by

J ADWAITH, 37
MUHAMMED ALTHAB H, 47
RAM GOPAL M P, 52
GOURI VINOD, 32

as part of the project based course

23EEJ303 : Digital Electronics and Logic Design

in partial fulfillment of the requirements for the award of the Degree
of
Bachelor of Technology
In
Electrical and Electronics Engineering



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

T.K.M. COLLEGE OF ENGINEERING, KOLLAM

NOVEMBER, 2024

ABSTRACT

The "Password Security System" is a hardware-based project designed to control access to a secure area or device by requiring the correct input sequence of digits or characters. It utilizes digital logic ICs, such as comparators, counters and logic gates, to process and verify the entered password. The system is typically designed to compare the entered password with a predefined sequence stored in the circuitry. If the correct password is entered, the system triggers an output, like unlocking a door or enabling a device. For each wrong attempt, the counter increments and gives an alarm when three incorrect attempts are made. The advantage of using logic ICs is that the system is reliable, resistant to tampering, and doesn't rely on software, making it more secure in certain applications.

Contents

Abstract	2
Contents	4
List of Figures	5
1 Introduction	1
1.1 Enhancing Security with Digital Electronics	1
2 Relevance of the Project	2
2.1 Introduction	2
2.1.1 Practical Applications	2
2.1.2 Educational Value	2
2.2 Conclusion	2
3 Methodology	3
3.1 Introduction	3
3.2 Circuit Diagram and Components Required	3
3.2.1 IC 4081	4
3.2.2 IC CD4069	4
3.2.3 IC 4011	5
3.2.4 IC 7446	5
3.2.5 IC 4027	6
3.2.6 555 timer IC	6
3.3 Conclusion	7
4 Results and Discussions	8
4.1 Introduction	8
4.2 Final output	8
4.3 Conclusion	8
5 ADC/DAC Based Project	10
5.1 R-2R Ladder	10

5.2	Methodology	12
5.2.1	Components Required and Circuit diagram	12
5.2.2	LM741 Op Amp	13
5.3	Results	13
Reference		14
Appendix		15

List of Figures

3.1	Circuit diagram	3
3.2	Pin out of IC 4081	4
3.3	Pin out of IC 4069	5
3.4	Pin out of IC 4011	5
3.5	Truth table for NAND	6
3.6	Pin out of IC 7446	6
3.7	Pin out of IC 4027	7
3.8	Pin out of 555 timer IC	7
4.1	Circuit	9
5.1	Circuit diagram	12
5.2	LM741 Pin diagram	13

Chapter 1

Introduction

In today's world, secure access control is essential to protect sensitive areas, devices, and data. A password security system based on digital electronics offers a reliable and tamper-resistant solution. Unlike software-based systems, which can be vulnerable to hacking or software malfunctions, a hardware-based password system uses digital logic ICs to verify password input.

This project utilizes basic digital electronics components—such as comparators, counters, and logic gates—to design a system that verifies a user-entered password against a predefined sequence. If the correct password is entered, an output is triggered, which could activate mechanisms like unlocking a door or enabling access to a device. Furthermore, the system incorporates a counter to track incorrect attempts, with an alarm activating if a maximum threshold is reached (e.g., three incorrect attempts).

This password security system project highlights the practical applications of digital electronics for secure access control, showcasing the simplicity and reliability that hardware-based solutions offer. It's particularly valuable for applications where software independence, reliability, and resilience to tampering are crucial.

1.1 Enhancing Security with Digital Electronics

In modern security systems, reliable access control is essential. The Password Security System leverages digital electronics to create a secure, tamper-resistant solution using components like comparators, counters, and logic gates. By relying on hardware rather than software, this system minimizes vulnerabilities and ensures dependable performance, making it ideal for protecting restricted areas or devices. This project showcases the effectiveness of digital electronics in building robust security systems.

Chapter 2

Relevance of the Project

2.1 Introduction

The Password Security System project is highly relevant in today's security-conscious world, where protecting sensitive areas and devices is crucial. By using digital electronics rather than software, this system provides enhanced tamper resistance and reliability, which are essential for applications where software vulnerabilities could pose security risks. Its hardware-based approach makes it suitable for environments that require dependable, standalone solutions, such as laboratories, data centers, and restricted facilities. Additionally, the project demonstrates practical applications of digital logic, making it valuable for students and professionals exploring secure access control in embedded systems.

2.1.1 Practical Applications

This system is useful in various real world settings including banks, Laboratories, server rooms, and other restricted areas. It showcases how digital electronics can provide robust access control without the need for Complex Software Solutions.

2.1.2 Educational Value

The project serves as a practical learning tool for students and beginners in digital electronics. It allows them to apply theoretical knowledge about comparators, counters and logic gates in a real world application strengthening their understanding of digital logic.

2.2 Conclusion

The Password Security System project shows how hardware can make secure systems more reliable and safer. By using digital electronics instead of software, it reduces risks of hacking and doesn't need frequent maintenance. This project is useful for learning about digital logic and provides a strong, simple way to control access in real-life situations.

Methodology

3.1 Introduction

The methodology for developing the Password Security System project in digital electronics involves a step-by-step approach to design and implement a secure access control mechanism using hardware components. This system relies on digital logic ICs, such as counters, comparators, and logic gates, to verify password entries without the need for software. The process includes setting up a keypad for password input, designing a circuit to compare the entered password with a stored sequence, and integrating feedback mechanisms like LED indicators and alarms. Each stage of development focuses on ensuring the system's accuracy, reliability, and security in various practical scenarios. The circuit, design etc. can be included in this chapter.

3.2 Circuit Diagram and Components Required

Circuit Diagram

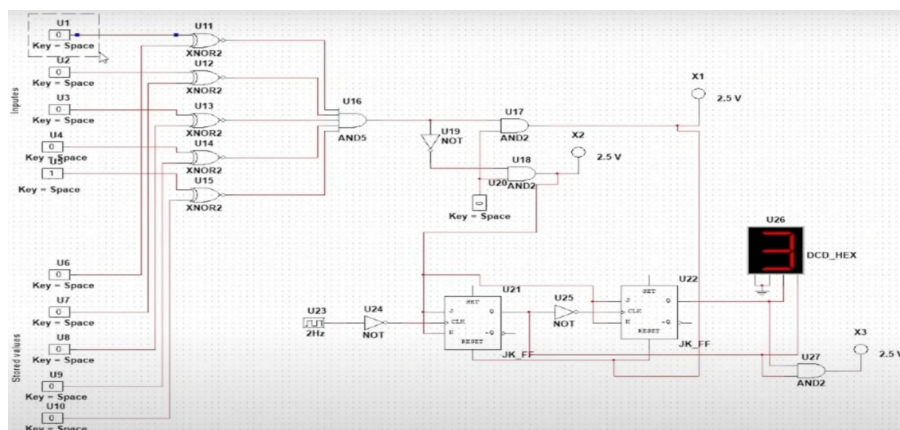


Figure 3.1: Circuit diagram

SI No.	Components	No.s
1	IC 4011 quad NAND gate	1
2	555 timer IC	1
3	4 position DIP switch	2
4	LED	2
5	5V Buzzer	1
6	IC CD4027B JK Flip Flop	1
7	IC 4011 quad NAND gate	1
8	IC CD4069 NOT gate	1
9	7 segment hex decoder	1
10	Push Button	1
11	IC 4081 Quad AND gate	1
12	9V battery	1
13	Breadboard	1
14	Connecting Wires	

3.2.1 IC 4081

The CD4081 is a four-AND gate CMOS chip. An AND gate is a logic gate that only outputs a HIGH value when all of its inputs are also HIGH. There are four AND gates in this Integrated Circuit (IC), each with two inputs. As a result, it's commonly referred to as a Quad 2-Input AND Gate.

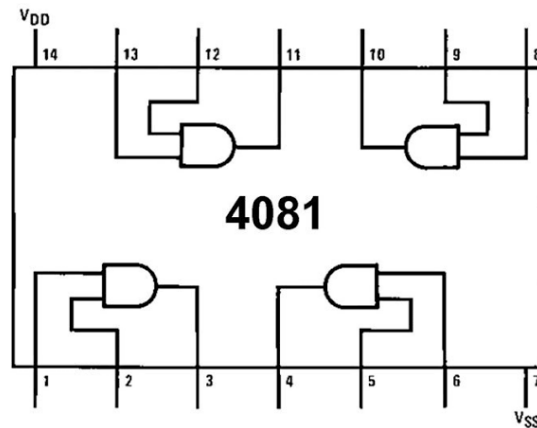


Figure 3.2: Pin out of IC 4081

3.2.2 IC CD4069

The CD4069 UB device consist of six CMOS inverter circuits. These devices are intended for all generalpurpose inverter applications where the mediumpower TTL-drive and logic-level-conversion capabilities of circuits such as the CD4009 and CD4049 hex inverter and buffers are not required.

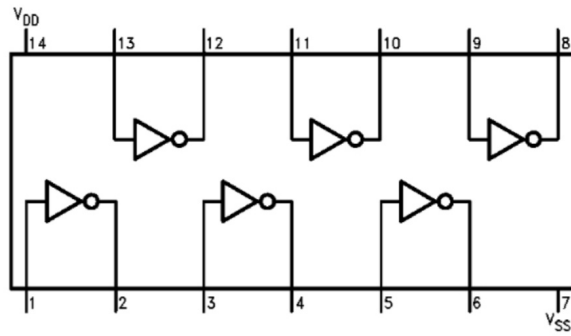


Figure 3.3: Pin out of IC 4069

3.2.3 IC 4011

The 4011 is a member of the 4000 Series CMOS range, and contains four independent NAND gates, each with two inputs. The pinout diagram, given on the right, is the standard two-input CMOS logic gate IC layout:

Pin 7 is the negative supply. Pin 14 is the positive supply. Pins 1 and 2, 5 and 6, 8 and 9, 12 and 13 are gate inputs. Pins 3, 4, 10, 11 are gate outputs.

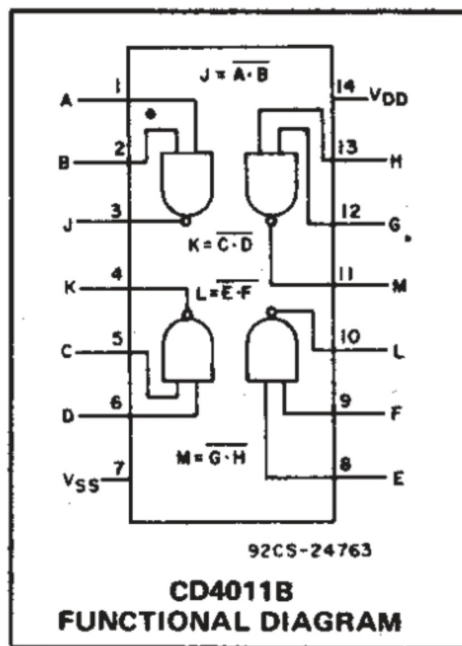


Figure 3.4: Pin out of IC 4011

3.2.4 IC 7446

Single BCD to 7-Segment Decoder Outputs Directly Interface to CMOS, NMOS and TTL. Large Operating Voltage Range. Wide Operating Conditions. Not Recommended for New Designs.

A	B	F
0	0	1
1	0	1
0	1	1
1	1	0

Figure 3.5: Truth table for NAND

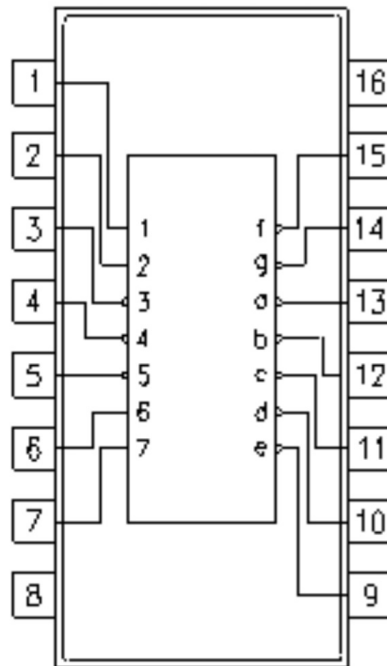


Figure 3.6: Pin out of IC 7446

3.2.5 IC 4027

CD4027B is a single monolithic chip integrated circuit containing two identical complementary-symmetry J-K flip flops. Each flip-flop has provisions for individual J, K, Set, Reset, and Clock input signals. Buffered Q and Q signals are provided as outputs. This input output arrangement provides for compatible operation with the RCA-CD 4013 B dual D-type flip-flop.

3.2.6 555 timer IC

Depending on the manufacturer, the standard 555 timer package includes 25 transistors, 2 diodes, and 15 resistors on a silicon chip installed in an 8-pin mini dual-in-line package (DIP-8). Variants consist of combining multiple chips on one board. However, 555 is still the most popular.

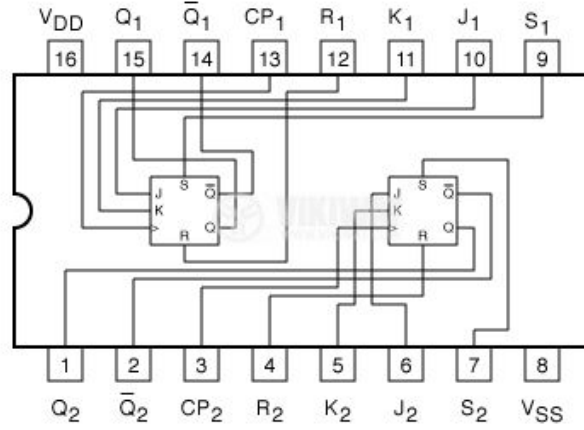


Figure 3.7: Pin out of IC 4027

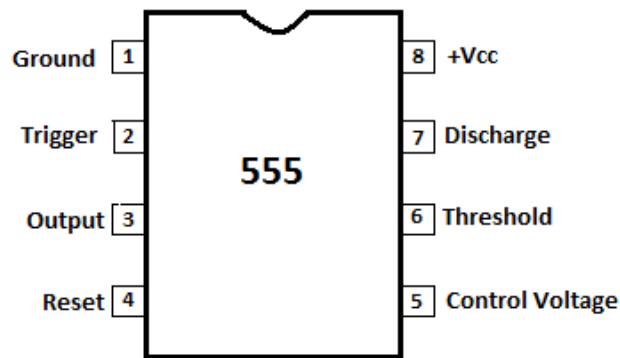


Figure 3.8: Pin out of 555 timer IC

3.3 Conclusion

The methodology behind the Password Security System project demonstrates the effectiveness of a structured, hardware-based approach to secure access control. By carefully designing each component—from password entry and verification to feedback mechanisms and error handling—the project achieves a reliable and tamper-resistant solution. This step-by-step method highlights the advantages of using digital electronics in security applications, offering a dependable, standalone system that is ideal for real-world environments requiring strong access control.

Chapter 4

Results and Discussions

4.1 Introduction

The Password Security System project successfully demonstrates a hardware-based approach to access control. Testing confirmed that the system accurately verifies the password entered and triggers appropriate responses, such as unlocking or an alarm, based on the input. The counter effectively tracks incorrect attempts, activating an alert after a set threshold, enhancing security.

The project's results highlight the reliability and stability of using digital ICs, with minimal risk of software-related vulnerabilities. In discussions, it's clear that while hardware-based systems are less flexible than software alternatives, they provide greater tamper resistance and simplicity, which can be valuable in high-security applications. Future improvements could include adding multi-level access or biometric verification to enhance security further.

4.2 Final output

The final output showcases the following key features:

Accurate Password Verification: Ensures that only authorized individuals gain access.

Tamper Resistance: A hardware-based design reduces risks associated with software vulnerabilities.

Reliable Alarm System: Activates after three failed attempts, providing an additional layer of security.

Low Maintenance and Standalone Operation: Requires minimal upkeep, making it suitable for secure environments.

4.3 Conclusion

The results of the Password Security System project demonstrate that a hardware-based approach effectively achieves secure access control. The system accurately verifies password entries, successfully triggers access for

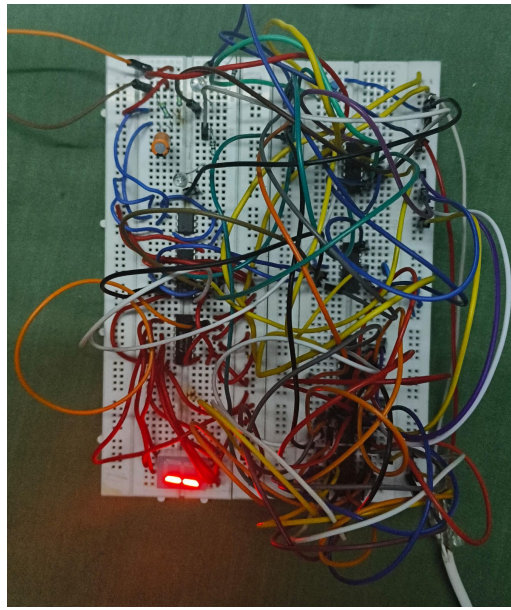
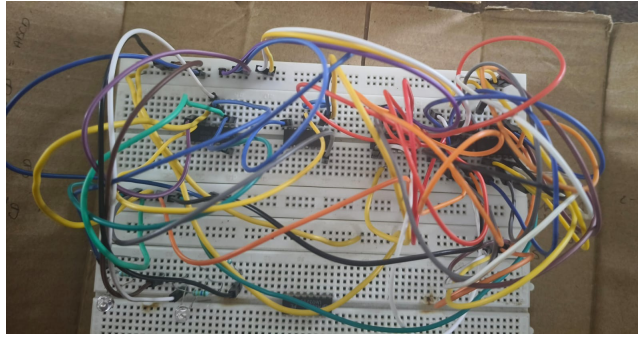


Figure 4.1: Circuit

correct inputs, and activates an alarm after multiple incorrect attempts, enhancing security. Testing confirms the system's reliability and simplicity, with minimal risk of tampering or software vulnerabilities. Overall, the project illustrates the strengths of using digital electronics for dependable and standalone security solutions, making it suitable for environments requiring robust access control.

Chapter 5

ADC/DAC Based Project

5.1 R-2R Ladder

The R-2R ladder DAC (Digital-to-Analog Converter) is a type of resistor network used to convert digital signals into analog signals. It's known for its simplicity and ease of implementation, especially when compared to other DAC architectures. Here's an overview of how it works and why it's often used:

1. Structure

The R-2R ladder DAC consists of a series of resistors arranged in an alternating pattern of values, R and 2R. The "ladder" name comes from its resemblance to a ladder, with two different resistor values connected in a repeating pattern.

2. Working Principle

Each input bit of the digital signal corresponds to a node in the resistor network. When a digital bit is set to '1', it allows current to pass through a specific path, and if it is set to '0', the path is bypassed. The current through each bit, determined by the resistor network, adds up to form the final analog output voltage. Due to the consistent R-2R arrangement, the output voltage is proportional to the weighted sum of the binary input bits.

3. Advantages

Simplicity and Scalability: R-2R networks only require two resistor values, which simplifies design and manufacturing.

Linearity: With ideal components, the R-2R ladder provides good linearity and accuracy.

Ease of Implementation: It's easy to expand to higher bit resolutions without changing resistor values, unlike binary-weighted DACs which require exponentially different resistor values.

4. Applications

Commonly used in audio and video DACs, digital signal processing, and microcontroller DACs due to its simplicity and effectiveness for moderate resolution requirements.

5. Limitations

Accuracy depends on resistor precision: Variations in resistor values can cause errors in the output.

Limited resolution: While good for many applications, it may not provide sufficient accuracy for very high-resolution DACs (e.g., 16-bit or above).

In essence, an R-2R ladder DAC is a straightforward, effective, and widely used solution for converting digital signals to analog outputs, especially useful in systems where simplicity and cost-effectiveness are priorities.

5.2 Methodology

5.2.1 Components Required and Circuit diagram

1. Resistors: Resistors with values of R and $2R$ (e.g., $R = 10k$, $2R = 20k$) are needed for the ladder network.
2. Op-amp: As a buffer (optional, but recommended for a stable output).
3. Breadboard and Jumper Wires: For assembling the circuit.
4. Power Supply: For providing stable voltage levels to the DAC circuit.
5. Multimeter: To measure and observe the output voltage.

1. Circuit Design

Understanding the R-2R Ladder Structure: Review the R-2R ladder structure, noting that it consists of a repeated sequence of R and $2R$ resistors in a ladder-like arrangement.

Schematic Creation: Draw a schematic diagram of the DAC circuit, showing each resistor and the corresponding digital input connected to it.

Determine Resistor Values: Choose suitable resistor values for R and $2R$ (e.g., $R = 10k$ and $2R = 20k$) to achieve the desired precision.

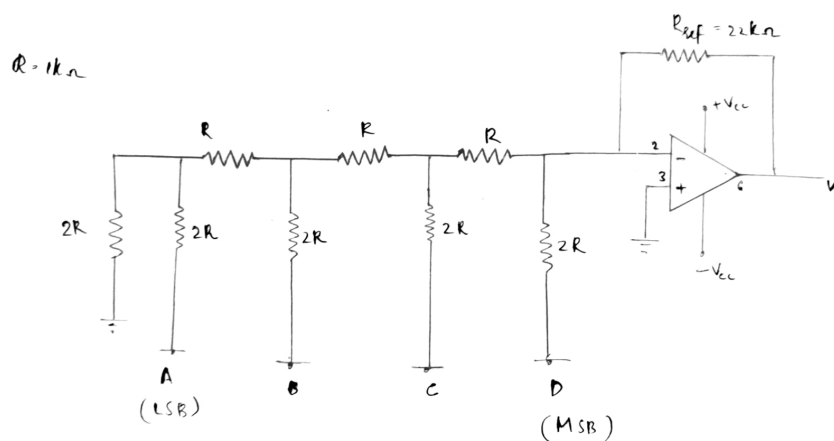


Figure 5.1: Circuit diagram

5.2.2 LM741 Op Amp

The LM741 series are general purpose operational amplifiers which feature improved performance over industry standards like the LM709. The amplifiers offer many features which make their application nearly foolproof: overload protection on the input and output, no latch-up when the common mode range is exceeded, as well as freedom from oscillation

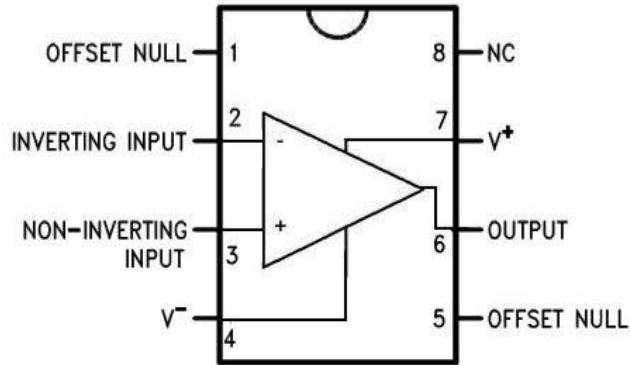


Figure 5.2: LM741 Pin diagram

5.3 Results

The output voltages were recorded for each binary input (e.g., 0000 to 1111 for a 4-bit DAC). The measured output values closely matched the expected theoretical values, indicating that the DAC successfully converted the digital inputs to analog voltages.

The R-2R Ladder DAC successfully converted digital signals to analog outputs with high accuracy and linearity. Minor errors observed were within acceptable tolerance levels, largely attributable to resistor precision. Overall, the R-2R ladder DAC design proved to be a cost-effective and efficient method for digital-to-analog conversion, with scalability for higher bit resolutions.

These findings validate the effectiveness of the R-2R ladder DAC in applications requiring moderate-resolution DACs, and the results align well with theoretical predictions for this type of circuit.

References

1. YouTube
2. www.subr.edu
3. www.scribd.com
4. ChatGPT

Appendix

1. Components List

Keypad, comparator ICs, counter ICs, logic gates, LED indicators, alarm module, breadboard, and power supply.

2. Circuit Diagram

Main circuit showing connections between keypad, comparator, counter, and LEDs, with an alarm circuit for incorrect attempts.

3. Flowchart of Operation

Password entry → comparison → correct/incorrect response → counter increment → alarm trigger after three incorrect attempts.

4. Testing Procedures

Test correct and incorrect password entries, counter function, and alarm activation after reaching the attempt limit.

5. Troubleshooting Tips

Verify power connections, component wiring, and IC placements if any part of the system malfunctions.